 


*@Sree Vishnu Varthini*

*Day - 6*

# *Embedded Systems Programming*

# ***SR FLIPFLOP***



An SR flip-flop, or Set-Reset flip-flop, is a basic memory element in digital electronics. It has two inputs: S (Set) and R (Reset), and two outputs: Q and Q' (the inverse of Q).

## ***Truth Table***

S	R	$Q_{n+1}$
0	0	$Q_n$ (No Change)
0	1	0
1	0	1
1	1	x

## ***Components of SR Flipflop:***

### **Inputs:**

- **S (Set):** Sets the output (Q) to 1.
- **R (Reset):** Resets the output (Q) to 0.

### **Outputs:**

- **Q:** Main output of the flip-flop.
- **Q':** Inverse of Q (if  $Q = 1$ , then  $Q' = 0$  and vice versa).

## ***Analogy:***

Imagine the SR flip-flop as a light switch:

- The Set input (S) turns the light **on** ( $Q = 1$ ).
- The Reset input (R) turns the light **off** ( $Q = 0$ ).
- When neither Set nor Reset is pressed ( $S = 0$ ,  $R = 0$ ), the light stays in whatever **state it was previously in**.
- If both buttons are pressed at the same time ( $S = 1$ ,  $R = 1$ ), the system is confused and enters an **invalid state**.


## ***Working:***

### **Case 1: Hold State ( $S = 0$ , $R = 0$ )**

Outputs of both NAND gates (N1 and N2) become 1.

Inputs of both NAND gates (N3 and N4) are 1, which results in depending on the previous Q values for output.

 The flip-flop remains in its current state, with Q and Q' retaining their previous values.



## ***Working:***

### **Case 2: Reset State ( $S = 0$ , $R = 1$ )**

$S = 0 \rightarrow$  Output of the first NAND gate (N1) becomes 1.


$R = 1 \rightarrow$  Output of the second NAND gate (N2) becomes 0.

Input to fourth NAND gate (N4) is 0 and so  $Q'$  becomes 1.

Due to this, input to third NAND (N3) gate becomes 1 and 1.

So  $Q$  becomes 0.

 $Q'$  is set to 1, and so  $Q$  is set to 0.



## ***Working:***

### **Case 3: Set State ( $S = 1, R = 0$ )**


$S = 1 \rightarrow$  Output of the first NAND gate (N1) becomes 0.

$R = 0 \rightarrow$  Output of the second NAND gate (N2) becomes 1.

Input to third NAND gate (N3) is 0 and so Q becomes 1.

Due to this, input to fourth NAND (N4) gate becomes 1 and 1. So  $Q'$  becomes 0.

 Q is set to 1, and so  $Q'$  is set to 0.



## ***Working:***

### **Case 4: Invalid State ( $S = 1, R = 1$ )**


$S = 1 \rightarrow$  Output of the first NAND gate (N1) becomes 0.

$R = 1 \rightarrow$  Output of the second NAND gate (N2) becomes 0.

Inputs to both NAND gates (N3 and N4) is 0.

So both outputs,  $Q$  and  $Q'$ , become 1, which is invalid since  $Q'$  should be the inverse of  $Q$ .

 This input should be avoided in practical designs.



@Sree Vishnu Varthini

***Was it  
helpful?  
follow for more!***

**P.S.** You can access the **Embedded Systems Programming** course by contacting **Balajee Seshadri** Sir through the WhatsApp number provided on his profile.



Like



Comment



Share



Save